

Dependent sources

This example showcases how ELABorate deals with circuits containing dependent sources.

Voltage-Controlled-Voltage-Sources

```
circuit = Circuit('circuits/E_src.txt');  
circuit.list
```

```
ans =  
      'V1 1 0 DC 12  
      R1 1 2 2000  
      R2 2 0 4000  
      R3 3 4 20000  
      C1 1 2 0.0001  
      C2 4 0 0.001  
      E1 3 2 1 2 100  
      '
```

```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.504304 sec).

```
circuit.symbolic_node_voltages
```

```
ans =  

$$\left( \begin{array}{l} v_1 = V_1 \\ v_2 = \frac{R_2 V_1 (C_1 R_1 s + C_2 R_3 s - C_2 E_1 R_1 s + C_1 C_2 R_1 R_3 s^2 + 1)}{\sigma_1} \\ v_3 = \frac{V_1 (C_2 R_3 s + 1) (R_2 + E_1 R_1 + C_1 R_1 R_2 s)}{\sigma_1} \\ v_4 = \frac{V_1 (R_2 + E_1 R_1 + C_1 R_1 R_2 s)}{\sigma_1} \end{array} \right)$$

```

where

$$\sigma_1 = R_1 + R_2 + C_1 R_1 R_2 s + C_2 R_1 R_2 s + C_2 R_1 R_3 s + C_2 R_2 R_3 s - C_2 E_1 R_1 R_2 s + C_1 C_2 R_1 R_2 R_3 s^2$$

```
TF = ELAB.ec2tf(circuit,1,3)
```

Numerical evaluation successful (0.168125 sec).
Transfer function object created successfully (1.922969e-01 sec).


```
TF =  

$$\frac{s^2 + 255.1 s + 12.75}{s^2 - 41.95 s + 0.375}$$

```

Continuous-time transfer function.

```
bode(TF)
```

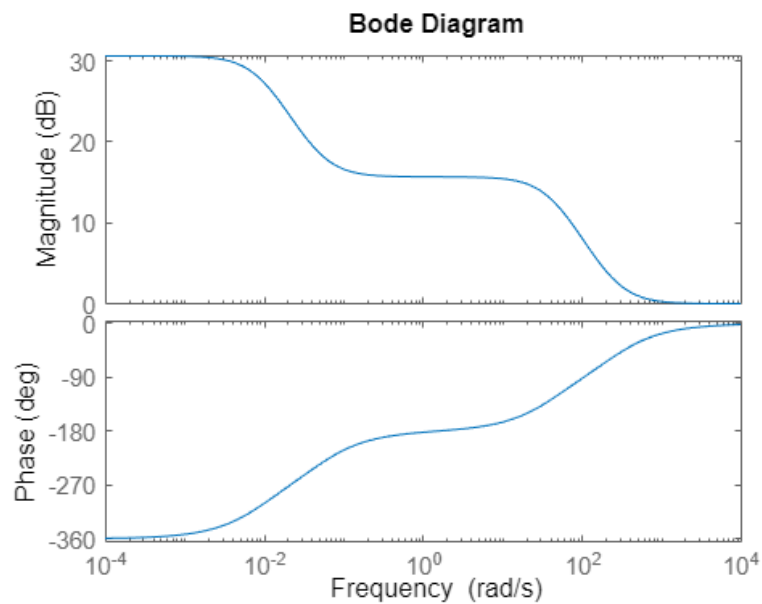

Voltage-Controlled-Current-Sources

```
circuit = Circuit('circuits/G_src.txt');
circuit.list
```

```
ans =
'V1 1 0 DC 12
R1 1 2 2000
R2 3 0 4000
R3 4 0 8000
L1 4 0 0.2
C1 2 3 0.001
G1 4 3 2 3 50
'
```

```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.393459 sec).

```
circuit.symbolic_node_voltages
```

```
ans =
```

$$\begin{pmatrix} v_1 = V_1 \\ v_2 = \frac{V_1 (G_1 R_2 + C_1 R_2 s + 1)}{\sigma_1} \\ v_3 = \frac{R_2 V_1 (G_1 + C_1 s)}{\sigma_1} \\ v_4 = -\frac{G_1 L_1 R_3 V_1 s}{(R_3 + L_1 s) \sigma_1} \end{pmatrix}$$

where

$$\sigma_1 = G_1 R_2 + C_1 R_1 s + C_1 R_2 s + 1$$

```
TF = ELAB.ec2tf(circuit,1,4)
```

Numerical evaluation successful (0.0932147 sec).


Transfer function object created successfully (1.176469e-01 sec).

TF =

$$\frac{-6.667e04 \text{ s}}{s^2 + 7.333e04 \text{ s} + 1.333e09}$$

Continuous-time transfer function.

```
bode(TF)
```

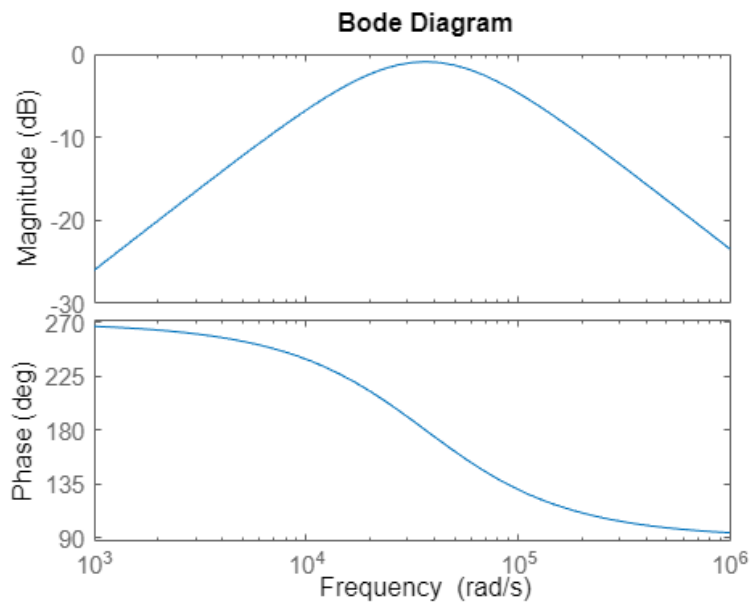

Current-Controlled-Voltage-Sources

```
circuit = Circuit('circuits/H_src.txt');
circuit.list
```

```
ans =
'V1 1 0 DC 12
R1 1 2 2000
R2 2 0 4000
L1 3 0 0.02
C1 3 0 0.0002
H1 3 2 V1 10
'
```

```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.482394 sec).

```
circuit.symbolic_node_voltages
```

```
ans =
```

$$\begin{pmatrix} v_1 = V_1 \\ v_2 = \frac{R_2 V_1 (C_1 H_1 L_1 s^2 + L_1 s + H_1)}{\sigma_1} \\ v_3 = -\frac{L_1 V_1 s (H_1 - R_2)}{\sigma_1} \end{pmatrix}$$

where

$$\sigma_1 = R_1 R_2 + H_1 R_2 + L_1 R_1 s + L_1 R_2 s + C_1 H_1 L_1 R_2 s^2 + C_1 L_1 R_1 R_2 s^2$$

```
TF = ELAB.ec2tf(circuit,1,3)
```


Numerical evaluation successful (0.120139 sec).
Transfer function object created successfully (1.810424e-01 sec).

```
TF =
```

$$\frac{2.481 \text{ s}}{s^2 + 3.731 \text{ s} + 2.5e05}$$

Continuous-time transfer function.

```
bode(TF)
```

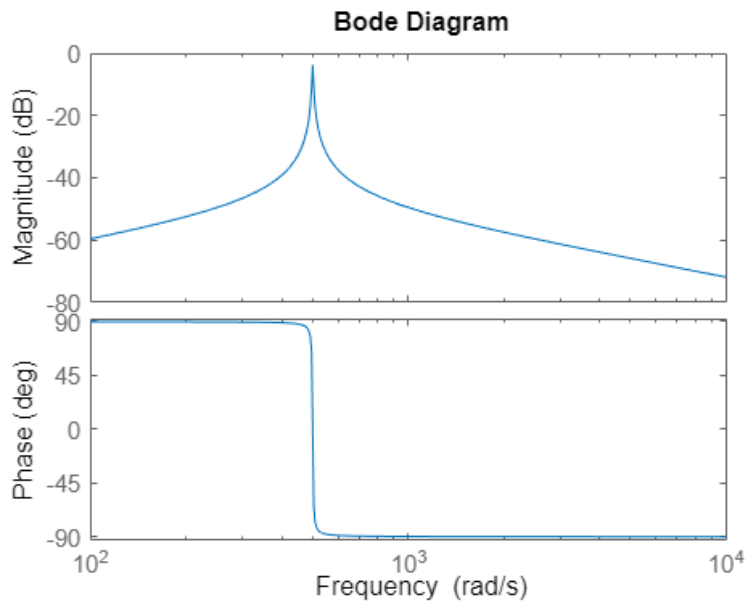

Current-Controlled-Current-Sources

```
circuit = Circuit('circuits/F_src.txt');
circuit.list
```

```
ans =
'V1 1 0 DC 12
R1 1 2 2000
R2 2 0 4000
R3 3 0 8000
L1 2 0 0.001
C1 3 0 0.000001
F1 3 2 V1 200
'
```

```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.411323 sec).

```
circuit.symbolic_node_voltages
```

```
ans =
```

$$\begin{pmatrix} v_1 = V_1 \\ v_2 = -\frac{L_1 R_2 V_1 s (F_1 - 1)}{R_1 R_2 + L_1 R_1 s + L_1 R_2 s - F_1 L_1 R_2 s} \\ v_3 = \frac{F_1 R_3 V_1 (R_2 + L_1 s)}{(C_1 R_3 s + 1) (R_1 R_2 + L_1 R_1 s + L_1 R_2 s - F_1 L_1 R_2 s)} \end{pmatrix}$$

```
TF = ELAB.ec2tf(circuit,1,3)
```

Numerical evaluation successful (0.108263 sec).
Transfer function object created successfully (1.477153e-01 sec).

```
TF =
```

$$\frac{-251.9 s - 1.008e09}{s^2 - 9951 s - 1.259e06}$$

Continuous-time transfer function.

bode(TF)

