


Simplifying circuits

ELAB can recursively simplify your circuit, updating the entire circuit object in the process.

We start by loading a circuit from a text file and displaying its netlist. This circuit is arbitrary and could be of any size, shape and constitution. The circuit is then analyzed and some results are displayed.

```
circuit = Circuit('circuits/complex.txt');  
circuit.list
```
 
```
ans =  
'I1 1 0 AC 5  
I2 1 0 AC 10  
R1 1 2 1000  
R2 2 0 2000  
R3 2 0 2000  
R4 1 2 3000  
R5 1 0 1000  
L1 3 1 0.02  
L2 3 0 0.03  
L3 1 0 0.2  
C1 1 0 0.000002  
C2 0 1 0.000003  
C3 1 0 0.00002  
,
```




```
ELAB.analyze(circuit)
```

Symbolic analysis successful (1.74678 sec).

As is apparent, there is unnecessary complexity to this circuit. We simplify the circuit and repeat the process. The circuit above has intentionally been constructed to simplify nicely for this example. Notice, that the naming and orientation of individual elements are accounted for.

```
ELAB.simplify(circuit);  
circuit.list
```
 
```
ans =  
'I_eq1 1 0 AC 15  
R_eq1 1 0 7000/11  
L_eq1 1 0 0.04  
C_eq1 1 0 0.000025  
,
```



ELAB recursively simplified the series and parallel resistors and capacitors, calculating their new values and giving them new names. Since all the resistors and capacitors can be reduced to a single resistor and capacitor in parallel, the node voltage at node 1 is simply the source voltage.

ELABorate can simplify series and parallels of any 2-terminal element.

```
ELAB.evaluate(circuit)
```

Symbolic analysis successful (0.158064 sec).

Numerical evaluation successful (0.0402752 sec).


```
TF = ELAB.sd2tf(rhs(circuit.numerical_node_voltages(1)))
```

TF =

$$\frac{-6e05 \text{ s}}{s^2 + 62.86 \text{ s} + 1e06}$$

Continuous-time transfer function.


```
bode(TF)
```

 

If the second parameter of the `simplify` function is set to `true`, the function will treat any resistor, capacitor or inductor as a generic impedance element, and it is therefore possible to simplify the three remaining passive elements to a single impedance element.

```
ELAB.simplify(circuit, true);
circuit.list
```
 
```
ans =
'Veq1 1 0 AC V1+V2
Zeq1 1 0 (7000.0*s)/(11.0*s+280.0*s^2+280000000.0)
'
```



The `simplify` function also works symbolically and even ensures appropriate naming of the new equivalent elements, even if the elements cannot be simplified down to a single element.

```
circuit = Circuit('circuits/multiple_eqs.txt');
circuit.list
```

```
ans =
'Vs 1 0 DC Vs
R1 1 2 R1
R2 2 3 R2
R3 4 5 R3
R4 4 5 R4
R5 5 0 R5
C1 3 4 C1
'
```

```
ELAB.simplify(circuit);
circuit.list
```

```
ans =
'Vs 1 0 DC Vs
Req1 2 1 R1+R2
Req2 3 0 R5+(R3*R4)/(R3+R4)
C1 2 3 C1
'
```

Here are some more examples.

```
circuit = Circuit('circuits/eq_impedance.txt');
circuit.list
```

```
ans =
'Vs 1 0 AC Vs
R1 2 3 3
R2 4 0 8
L1 2 4 0.2
```

```
C1 1 2 0.002
C2 3 0 0.01
,
```

```
ELAB.evaluate(circuit)
```

Symbolic analysis successful (0.502269 sec).

Numerical evaluation successful (0.211514 sec).

```
ELAB.simplify(circuit, true);
circuit.list
```

```
ans =
  'Vs 1 0 AC Vs
  Zeq1 1 0 0.002*s+(2405.0*s+8.0*s^2+1500.0)/(1100.0*s+s^2+500.0)
,
```

```
circuit = Circuit('circuits/triple_parallel.txt');
circuit.list
```

```
ans =
  'Vs 1 0 DC 12
  R1 1 0 3000
  R2 1 0 4000
  R3 1 0 2000
,
```

```
ELAB.simplify(circuit);
circuit.list
```

```
ans =
  'Vs 1 0 DC 12
  Req1 1 0 12000/13
,
```

```
circuit = Circuit('circuits/n_series.txt');
circuit.list
```

```
ans =
  'Vs 1 0 DC 12
  R1 1 2 3000
  R2 2 3 4000
  R3 3 0 2000
,
```

```
ELAB.simplify(circuit);
circuit.list
```

```
ans =
  'Vs 1 0 DC 12
  Req1 1 0 9000
,
```

```
circuit = Circuit('circuits/quad_series.txt');
circuit.list
```

```
ans =  
  'Vs 1 0 DC 12  
    R1 1 2 3000  
    R2 2 3 4000  
    R3 3 4 2000  
    R4 4 0 1000  
,
```

```
ELAB.simplify(circuit);  
circuit.list
```

```
ans =  
  'Vs 1 0 DC 12  
    Req1 1 0 10000  
,
```