

Resistor-Inductor-Capacitor circuits

1. Series RLC

```
circuit = Circuit('circuits/passive/c6_rlc_series.txt');  
circuit.list
```

```
ans =  
  'Vin 1 0 DC 5  
   R1 3 0 1000  
   L1 1 2 1  
   C1 2 3 0.0001  
   '
```

```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.272047 sec).

Say, you want expressions for node voltages.

```
circuit.symbolic_node_voltages
```

```
ans =  

$$\begin{pmatrix} v_1 = V_{in} \\ v_2 = \frac{V_{in} (C_1 R_1 s + 1)}{C_1 L_1 s^2 + C_1 R_1 s + 1} \\ v_3 = \frac{C_1 R_1 V_{in} s}{C_1 L_1 s^2 + C_1 R_1 s + 1} \end{pmatrix}$$

```

From the circuit, you can easily create a transfer function object, only giving the input and output nodes.

```
TF = ELAB.ec2tf(circuit, 1, 3)
```

Numerically evaluating circuit.

Numerical evaluation successful (0.0690117 sec).

Transfer function object created successfully (1.002254e-01 sec).


```
TF =
```

```
      1000 s  
-----  
s^2 + 1000 s + 10000
```


Continuous-time transfer function.

Matlab can then be used to visualize the circuit behavior as with any other system. Plotting the Bode diagram, we see that this circuit acts as a band-pass-filter.

```
bode(TF)
```

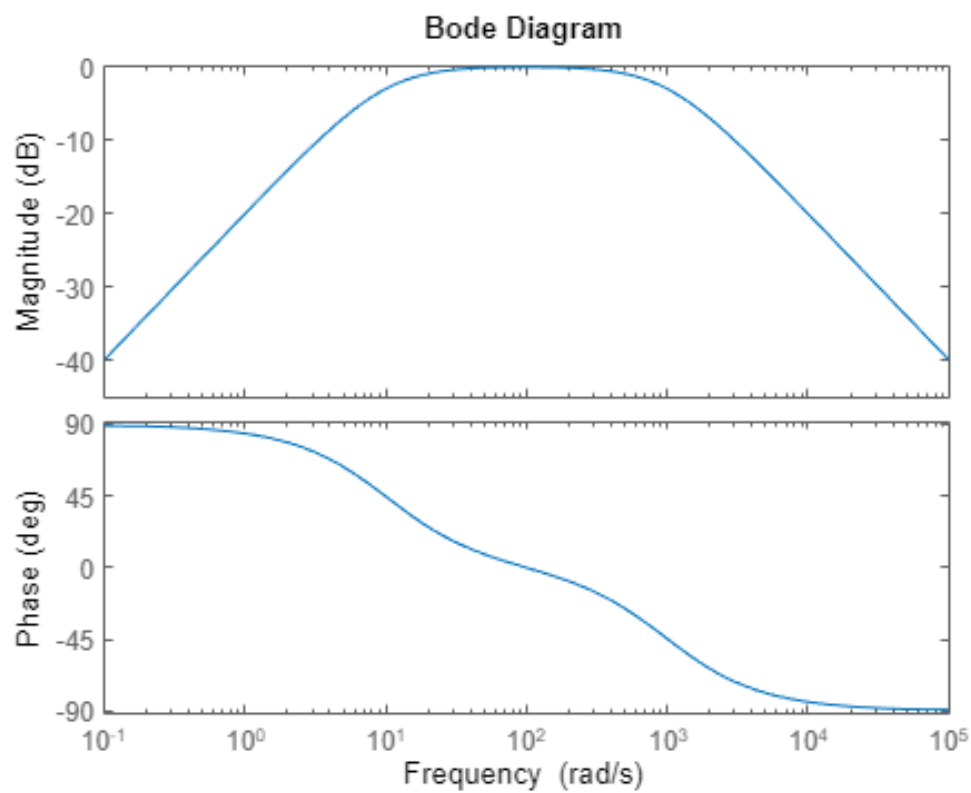

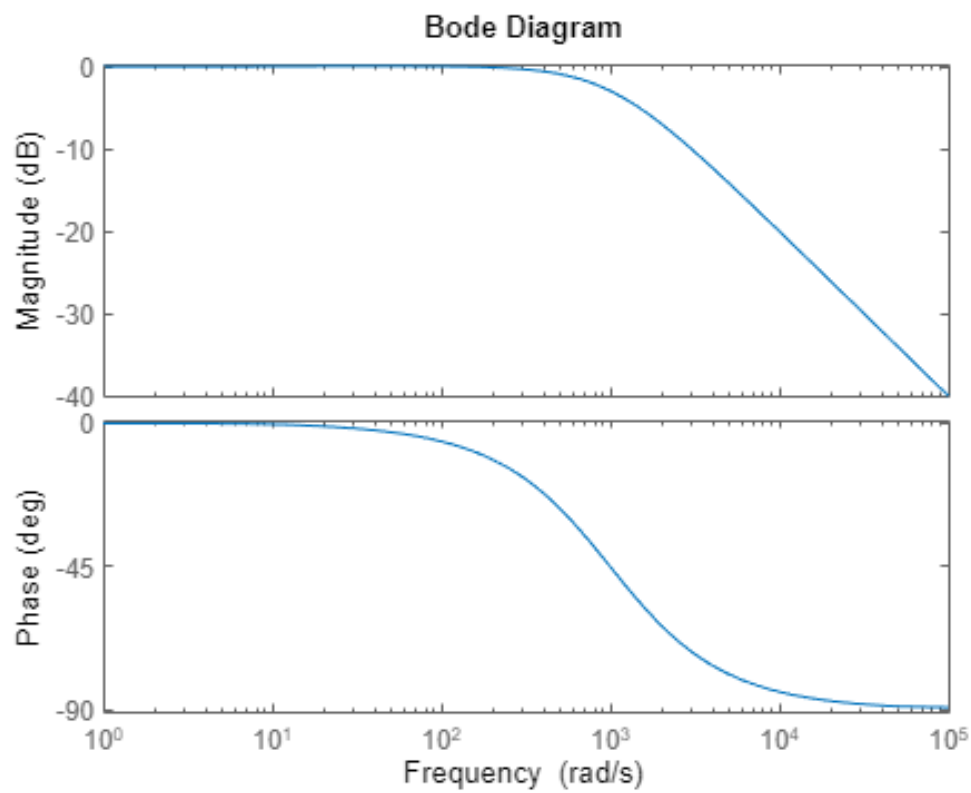Transfer function object created successfully (2.338730e-02 sec).



2. Parallel RLC

We can repeat the process to look at RLC in parallel.

```
circuit = Circuit('circuits/passive/c7_rlc_parallel.txt');  
circuit.list
```

```
ans =  
  'Iin 1 0 DC 2  
   R1 1 0 1000  
   L1 1 0 1  
   C1 1 0 0.0001  
'
```

```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.166269 sec).

```
ELAB.evaluate(circuit)
```

Numerical evaluation successful (0.0415356 sec).

In this case, because there is only one node besides ground, the transfer function is just the voltage at node 1.

```
circuit.numerical_node_voltages(1)
```


```
ans =  

$$v_1 = -\frac{2000 s}{\frac{s^2}{10} + s + 1000}$$

```

You can of course input the equation directly into Matlab's transfer function. Plotting the Bode diagram show that this is another kind of band-pass-filter.
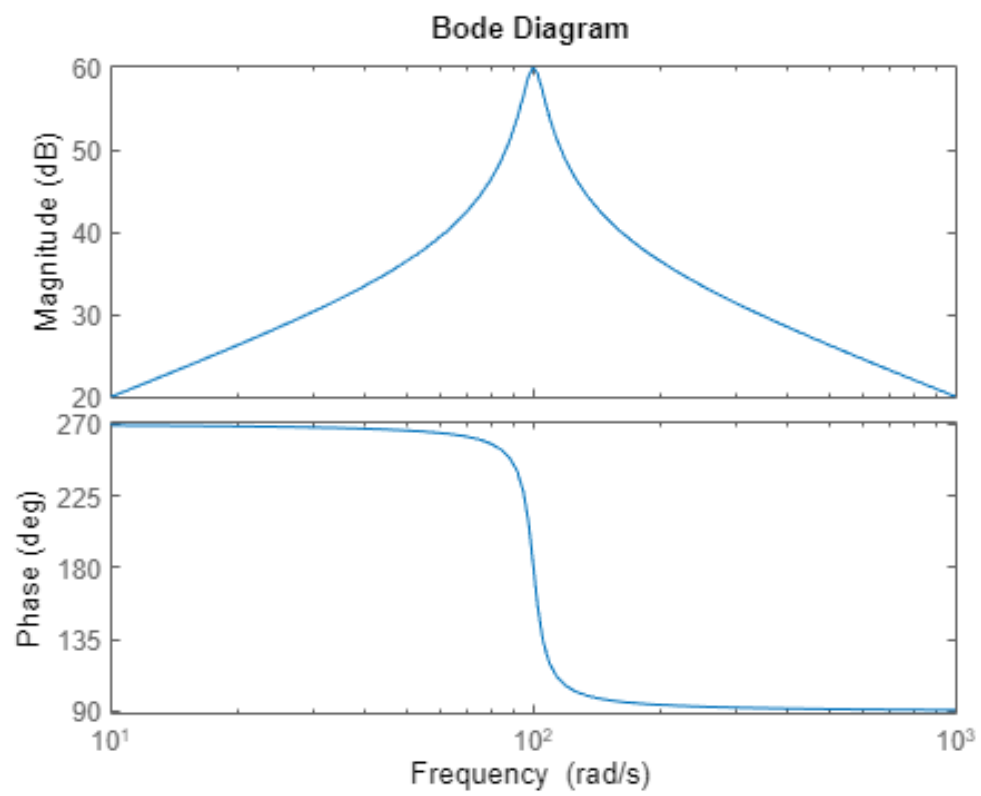
```
s = tf('s');  
TF = -(1000*s)/(s^2/10 + s + 1000);  
bode(TF)
```



Feel free to try any combination of resistors, capacitors and inductors.