

Simplifying circuits

ELAB can recursively simplify your circuit, updating the entire circuit object in the process.

We start by loading a circuit from a text file and display its netlist. The circuit is then analyzed and some results are displayed.

```
circuit = Circuit('circuits/passive/c9_series_parallel.txt');  
circuit.list
```

```
ans =  
'V1 1 0 AC 10  
R1 1 2 1000  
R2 2 0 2000  
R3 2 0 2000  
R4 1 2 3000  
R5 1 0 1000  
C1 1 0 2  
C2 0 1 3  
,
```

```
ELAB.analyze(circuit)
```

```
Symbolic analysis successful (0.400378 sec).
```

```
circuit.symbolic_node_voltages
```

```
ans =  

$$\begin{pmatrix} v_1 = V_1 \\ v_2 = \frac{R_2 R_3 V_1 (R_1 + R_4)}{R_1 R_2 R_3 + R_1 R_2 R_4 + R_1 R_3 R_4 + R_2 R_3 R_4} \end{pmatrix}$$

```

We then simplify the circuit and repeat the process.

```
ELAB.simplify(circuit);  
circuit.list
```

```
ans =  
'V1 1 0 AC 10  
Req1 1 0 7000/11  
Ceq1 1 0 5  
,
```

ELAB recursively simplified the series and parallel resistors and capacitors, calculating their new values and giving them new names. Since all the resistors and capacitors can be reduced to a single resistor and capacitor in parallel, the node voltage at node 1 is simply the source voltage.

```
ELAB.analyze(circuit)
```

```
Symbolic analysis successful (0.13938 sec).
```

```
circuit.symbolic_node_voltages
```

```
ans =  $v_1 = V_1$ 
```