


Simplifying circuits

ELAB can recursively simplify your circuit, updating the entire circuit object in the process.

We start by loading a circuit from a text file and displaying its netlist. This circuit is arbitrary and could be of any size and shape. The circuit is then analyzed and some results are displayed.

```
circuit = Circuit('circuits/series_parallel.txt');  
circuit.list
```
 
```
ans =  
'V1 1 0 AC 10  
R1 1 2 1000  
R2 2 0 2000  
R3 2 0 2000  
R4 1 2 3000  
R5 1 0 1000  
C1 1 0 2  
C2 0 1 3  
,
```



```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.414235 sec).

```
circuit.symbolic_node_voltages
```

```
ans =  


$$\begin{pmatrix} v_1 = V_1 \\ v_2 = \frac{R_2 R_3 V_1 (R_1 + R_4)}{R_1 R_2 R_3 + R_1 R_2 R_4 + R_1 R_3 R_4 + R_2 R_3 R_4} \end{pmatrix}$$

```

We then simplify the circuit and repeat the process. Notice, that the naming and orientation of individual elements are accounted for.

```
ELAB.simplify(circuit);  
circuit.list
```
 
```
ans =  
'V1 1 0 AC 10  
Req1 1 0 7000/11  
Ceq1 1 0 5  
,
```



ELAB recursively simplified the series and parallel resistors and capacitors, calculating their new values and giving them new names. Since all the resistors and capacitors can be reduced to a single resistor and capacitor in parallel, the node voltage at node 1 is simply the source voltage.

```
ELAB.analyze(circuit)
```

```
Symbolic analysis successful (0.143488 sec).
```

```
circuit.symbolic_node_voltages
```

```
ans = v1 = Vs
```

Let's check if it was done right. From the pre-simplify diagram, we see that the resistors simplify to:

$$\begin{aligned}
 R_{eq1} &= ((R_1 || R_4) + (R_2 || R_3)) || R_5 \\
 &= \left(\left(\frac{1k\Omega \cdot 3k\Omega}{1k\Omega + 3k\Omega} \right) + \left(\frac{2k\Omega \cdot 2k\Omega}{2k\Omega + 2k\Omega} \right) \right) \cdot 1k\Omega \\
 &= \frac{\left(\left(\frac{1k\Omega \cdot 3k\Omega}{1k\Omega + 3k\Omega} \right) + \left(\frac{2k\Omega \cdot 2k\Omega}{2k\Omega + 2k\Omega} \right) \right) + 1k\Omega}{1} \\
 &= 7k\Omega/11
 \end{aligned}$$

And the capacitors simplify to:

$$\begin{aligned}
 C_{eq1} &= C_1 || C_2 \\
 &= C_1 + C_2 \\
 &= 5
 \end{aligned}$$

ELABorate can simplify series and parallels of any 2-terminal element.

Here are examples of how a larger number of series and parallels are handled.

```
circuit = Circuit('circuits/triple_parallel.txt');
circuit.list
```

```
ans =
    'Vs 1 0 DC 12
    R1 1 0 3000
    R2 1 0 4000
    R3 1 0 2000
    '
```

```
ELAB.simplify(circuit);
circuit.list
```

```
ans =
```

```
'Vs 1 0 DC 12
Req1 1 0 12000/13
'
```

```
circuit = Circuit('circuits/triple_series.txt');
circuit.list
```

```
ans =
'Vs 1 0 DC 12
R1 1 2 3000
R2 2 3 4000
R3 3 0 2000
'
```

```
ELAB.simplify(circuit);
circuit.list
```

```
ans =
'Vs 1 0 DC 12
Req1 1 0 9000
'
```

```
circuit = Circuit('circuits/quad_series.txt');
circuit.list
```

```
ans =
'Vs 1 0 DC 12
R1 1 2 3000
R2 2 3 4000
R3 3 4 2000
R4 4 0 1000
'
```

```
ELAB.simplify(circuit);
circuit.list
```

```
ans =
'Vs 1 0 DC 12
Req1 1 0 10000
'
```

The simplify function also ensures appropriate naming of the new equivalent elements, even if the elements cannot be simplified down to one element.

```
circuit = Circuit('circuits/multiple_eqs.txt');
circuit.list
```

```
ans =
'Vs 1 0 DC Vs
R1 1 2 R1
R2 2 3 R2
R3 4 5 R3
R4 4 5 R4
R5 5 0 R5
C1 3 4 C1
'
```

```
ELAB.simplify(circuit);
circuit.list
```

```
ans =  
'Vs 1 0 DC Vs  
Req1 1 2 R1 + R2  
Req2 3 0 R5 + (R3*R4)/(R3 + R4)  
C1 2 3 C1  
,
```