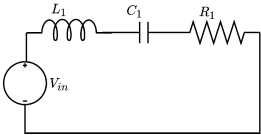


Resistor-Inductor-Capacitor circuits

1. Series RLC

```
circuit = Circuit('circuits/passive/c6_rlc_series.txt');  
circuit.list
```

```
ans =  
'Vin 1 0 DC 5  
R1 3 0 1000  
L1 1 2 1  
C1 2 3 0.0001  
,
```



```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.382394 sec).

Say, you want expressions for node voltages.

```
circuit.symbolic_node_voltages
```

```
ans =  

$$\begin{pmatrix} v_1 = \text{Vin} \\ v_2 = \frac{\text{Vin} (C_1 R_1 s + 1)}{C_1 L_1 s^2 + C_1 R_1 s + 1} \\ v_3 = \frac{C_1 R_1 \text{Vin} s}{C_1 L_1 s^2 + C_1 R_1 s + 1} \end{pmatrix}$$

```

From the circuit, you can easily create a transfer function object, only giving the input and output nodes.

```
TF = ELAB.ec2tf(circuit, 1, 3)
```

Numerically evaluating circuit.

Numerical evaluation successful (0.109854 sec).

Transfer function object created successfully (4.412587e-01 sec).


```
TF =
```

$$\frac{1000 s}{s^2 + 1000 s + 10000}$$

Continuous-time transfer function.

Matlab can then be used to visualize the circuit behavior as with any other system. Plotting the Bode diagram, we see that this circuit acts as a band-pass-filter.

```
bode(TF)
```

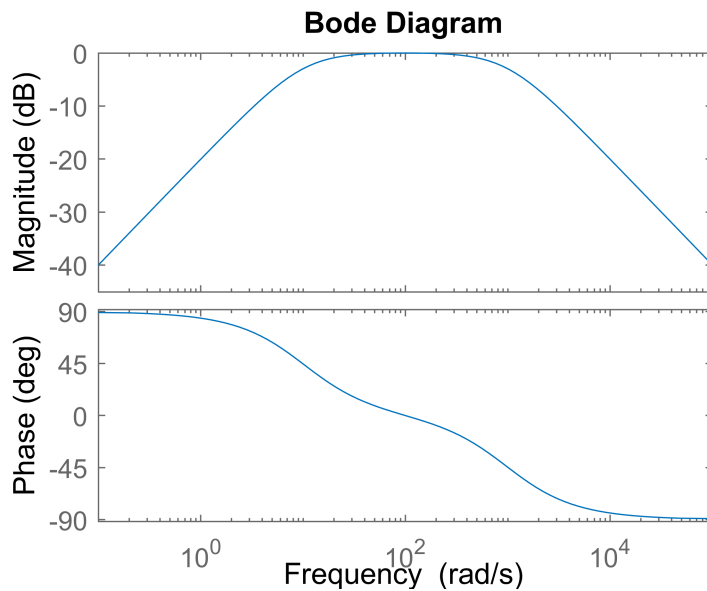


2. Parallel RLC

We can repeat the process to look at RLC in parallel.

```
circuit = Circuit('circuits/passive/c7_rlc_parallel.txt');
circuit.list
```
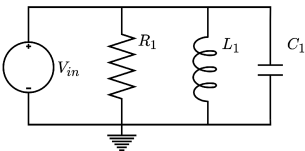
```
ans =
'Iin 1 0 DC 2
R1 1 0 1000
L1 1 0 1
C1 1 0 0.0001
'
```



```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.297009 sec).

```
ELAB.evaluate(circuit)
```

Numerical evaluation successful (0.0579531 sec).


In this case, because there is only one node besides ground, the transfer function is just the voltage at node 1.

```
circuit.numerical_node_voltages(1)
```

```
ans =
v1 = -  $\frac{2000 s}{\frac{s^2}{10} + s + 1000}$ 
```

You can of course input the equation directly into Matlab's transfer function. Plotting the Bode diagram show that this is another kind of band-pass-filter.
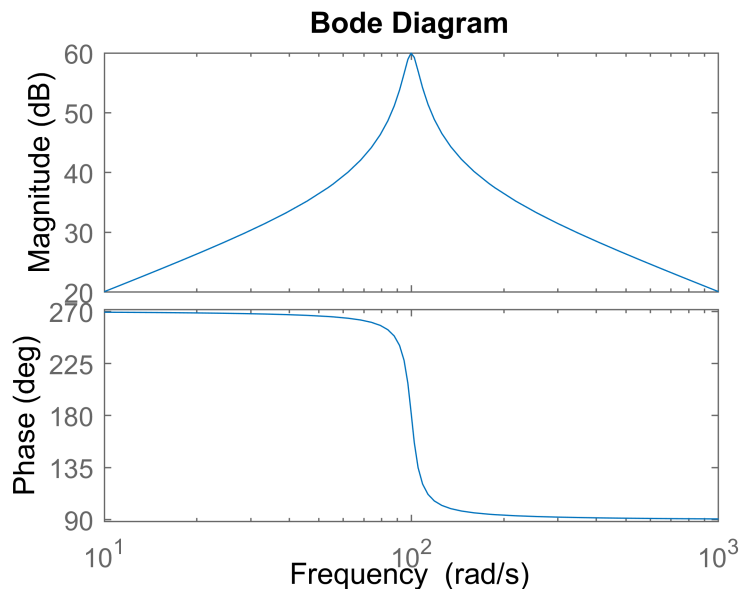
```
s = tf('s');  
TF = -(1000*s)/(s^2/10 + s + 1000);  
bode(TF)
```



Feel free to try any combination of resistors, capacitors and inductors.