

```
circuit = Circuit('circuits/thevenin.txt');
circuit.list
```

```
ans =
'V1 1 0 DC 28
V2 3 0 DC 7
R1 1 2 4
R2 2 0 2
R3 2 3 1
'
```

```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.340513 sec).

```
circuit.symbolic_node_voltages
```

```
ans =

$$\begin{pmatrix} v_1 = V_1 \\ v_2 = \frac{R_2 (R_1 V_2 + R_3 V_1)}{R_1 R_2 + R_1 R_3 + R_2 R_3} \\ v_3 = V_2 \end{pmatrix}$$

```

```
ELAB.evaluate(circuit)
```

Numerical evaluation successful (0.0430766 sec).

```
circuit.open(circuit.Resistors(2))
circuit.list
```

```
ans =
'V1 1 0 DC 28
V2 3 0 DC 7
R1 1 2 4
R3 2 3 1
'
```

```
ELAB.evaluate(circuit)
```

Symbolic analysis successful (0.256226 sec).

Numerical evaluation successful (0.0625652 sec).

```
circuit.symbolic_node_voltages
```

```
ans =

$$\begin{pmatrix} v_1 = V_1 \\ v_2 = \frac{R_1 V_2 + R_3 V_1}{R_1 + R_3} \\ v_3 = V_2 \end{pmatrix}$$

```

```
circuit.numerical_node_voltages
```

```
ans =
```

$$\begin{pmatrix} v_1 = 28 \\ v_2 = \frac{56}{5} \\ v_3 = 7 \end{pmatrix}$$

56/5

ans = 11.2000

1. Open-circuit the load element.
2. Analyze the circuit. Find voltage across the open gap.
3. Short-circuit voltage sources and open-circuit current sources.
4. Simplify to single resistor.
- 5.

```
circuit = Circuit('circuits/thevenin.txt');
ELAB.thevenin(circuit, circuit.Resistors(2));
```

Symbolic analysis successful (0.248778 sec).

Numerical evaluation successful (0.0430036 sec).

```
circuit = Circuit('circuits/thevenin.txt');
circuit.list
```

```
ans =
    'V1 1 0 DC 28
    V2 3 0 DC 7
    R1 1 2 4
    R2 2 0 2
    R3 2 3 1
    '
```

```
ELAB.thevenin(circuit, circuit.Resistors(2));
```

Symbolic analysis successful (0.235355 sec).

Numerical evaluation successful (0.0373992 sec).

```
circuit.list
```

```
ans =
    'Req1 0 1 4/5
    '
```

```
ELAB.simplify(circuit);
circuit.list
```

```
ans =
    'Req1 0 1 4/5
    '
```

```
circuit.Resistors(1)
```

```
ans =
```

Resistor with properties:

```
resistance: 4/5
impedance: 4/5
  anode: 0
  cathode: 1
  v_across: []
  i_through: []
num_terminals: 2
      id: 'Req1'
terminals: [0 1]
```