


Operational amplifier circuits

1. Simple inverting op-amp

The ideal operational amplifier is supported as a 3-terminal element. Let's see how the program handles circuits with OpAmps included. The analysis is done as with any other circuit.

```
circuit = Circuit('circuits/r_op_amp.txt');  
circuit.list
```
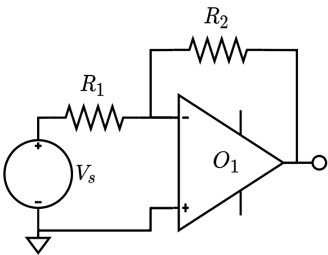
```
ans =  
'Vs 1 0 AC Vs  
R1 1 2 R1  
R2 2 3 R2  
O1 0 2 3  
,
```



```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.210827 sec).

```
circuit.symbolic_node_voltages
```

```
ans =  

$$\begin{pmatrix} v_1 = V_s \\ v_2 = 0 \\ v_3 = -\frac{R_2 V_s}{R_1} \end{pmatrix}$$


```

2. Inverting op-amp with additional reactive elements.

This is a slightly more complex example. We are still dealing with an inverting amplifier configuration.

```
circuit = Circuit('circuits/rc_op_amp.txt');  
circuit.list
```
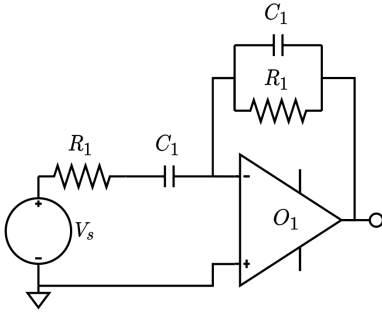
```
ans =  
'Vs 1 0 AC Vs  
R1 1 2 20000  
R2 3 4 20000  
C1 2 3 C1  
C2 3 4 C2  
O1 0 3 4  
,
```



Suppose we want to know what values for the capacitors, we need to choose, to achieve poles at $p_1 = -1000 \text{ rad/s}$ and $p_2 = -5000 \text{ rad/s}$.

```
ELAB.ec2sd(circuit,1,4)
```

Symbolic analysis successful (0.383169 sec).

Symbolic transfer function calculated successfully (3.916859e-01 sec).

ans =

$$\frac{v_4}{v_1} = -\frac{C_1 R_2 s}{(C_1 R_1 s + 1)(C_2 R_2 s + 1)}$$

From this transfer function, it is immediately apparent, that if $R_1 = R_2 = 20k\Omega$, then $C_1 = 1/1000R_1 = 0.05\mu F$ and $C_2 = 1/5000 = 0.01\mu F$.

```
circuit.Capacitors(1).capacitance = 0.05e-6;
```

ans = 5.0000e-08

```
circuit.Capacitors(2).capacitance = 0.01e-6;
```

```
circuit = Circuit('circuits/rc_op_amp_num.txt');
TF = ELAB.ec2tf(circuit,1,4)
```

Symbolic analysis successful (0.350098 sec).

Numerical evaluation successful (0.0874597 sec).


Transfer function object created successfully (1.211225e-01 sec).

TF =

$$\frac{-5000 s}{s^2 + 6000 s + 5e06}$$


Continuous-time transfer function.

```
pzmap(TF); grid on;
```

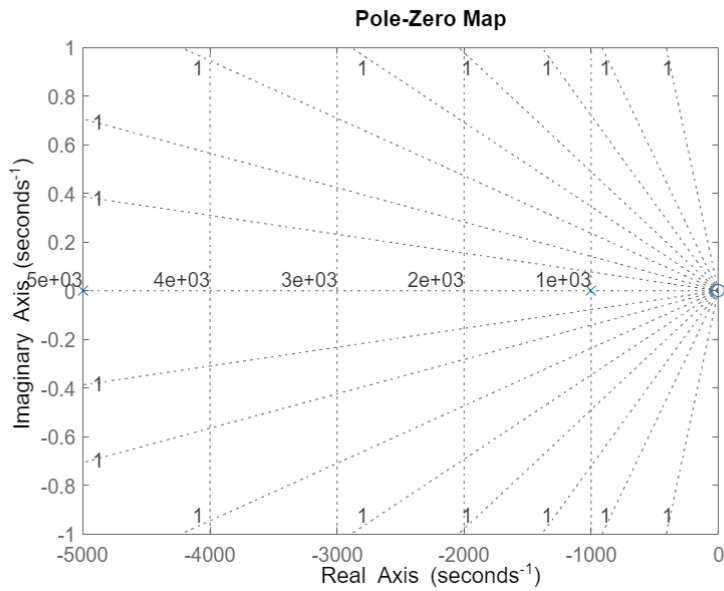

```
circuit = Circuit('circuits/state_variable_filter.txt');
circuit.list
```
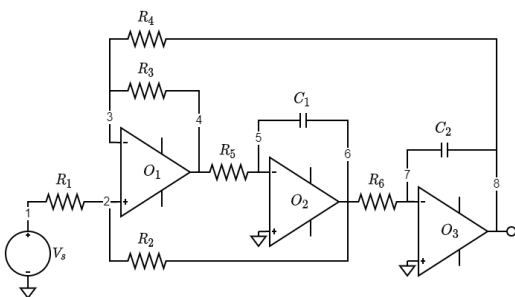
```
ans =
  'Vs 1 0 AC Vs
  R1 1 2 1000
  R2 2 6 19000
  R3 3 4 10000
  R4 3 8 10000
  R5 4 5 16000
  R6 6 7 16000
  C1 5 6 0.00000001
  C2 7 8 0.00000001
  O1 2 3 4
  O2 0 5 6
  O3 0 7 8
  '
```



```
bode(ELAB.ec2tf(circuit,1,4)); grid on; hold on;
```

Symbolic analysis successful (1.07754 sec).

Numerical evaluation successful (0.241102 sec).


Transfer function object created successfully (2.675553e-01 sec).

```
bode(ELAB.ec2tf(circuit,1,6));
```

Transfer function object created successfully (2.028830e-02 sec).

```
bode(ELAB.ec2tf(circuit,1,8)); hold off;
```

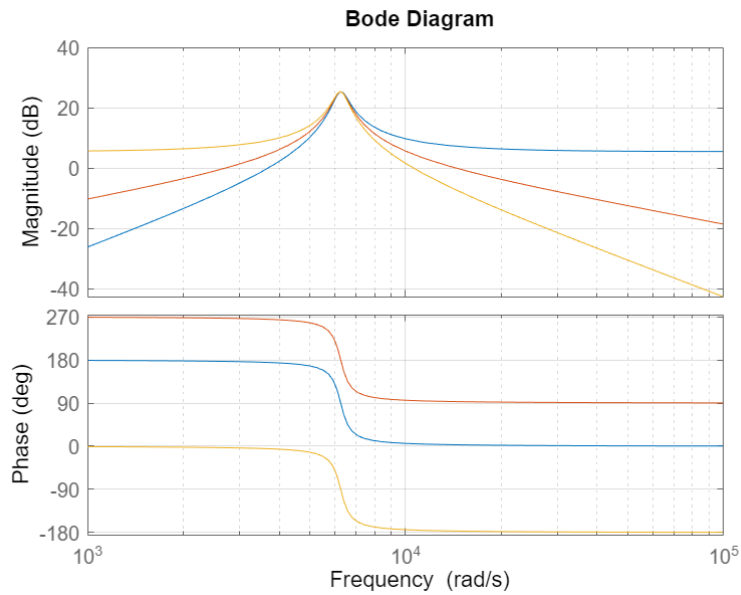Transfer function object created successfully (1.757560e-02 sec).



```
ELAB.ec2sd(circuit,1,8)
```

Symbolic transfer function calculated successfully (5.072700e-03 sec).

ans =

$$\frac{v_8}{v_1} = \frac{R_2 (R_3 + R_4)}{R_1 R_3 + R_2 R_3 + C_2 R_1 R_3 R_6 s + C_2 R_1 R_4 R_6 s + C_1 C_2 R_1 R_4 R_5 R_6 s^2 + C_1 C_2 R_2 R_4 R_5 R_6 s^2}$$