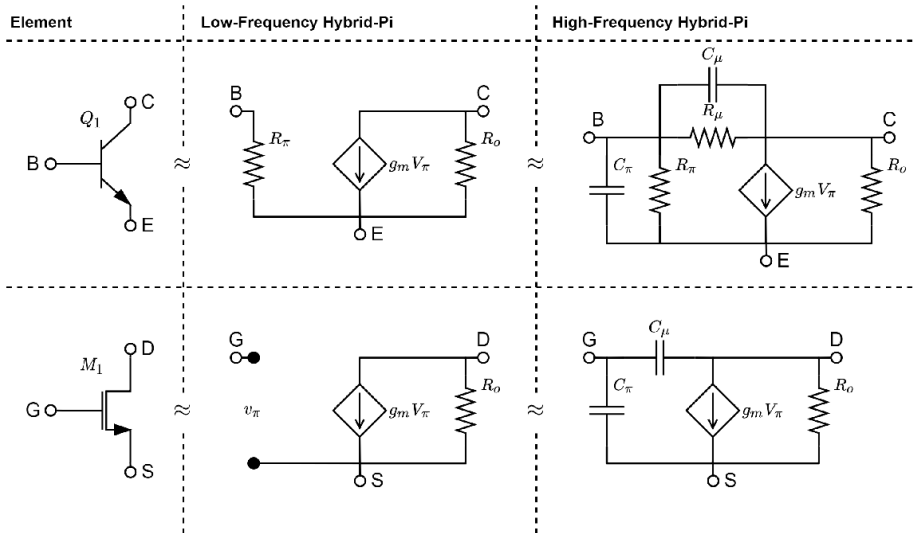


Transistor circuits

ELABorate can handle transistors by modelling them using an appropriate set of linear elements.




1. BJTs

We start by loading in a circuit containing a BJT. In this case, it's a simple common-source amplifier with biasing. The circuit is from Microelectronic Circuits 7th edition, page 410.

```
circuit = Circuit('circuits/bjt_cs_amp.txt');
circuit.list
```
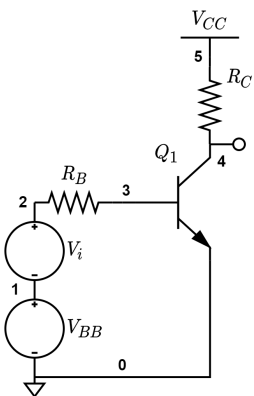
```
ans =
'V_BB 1 0 DC V_BB
V_CC 5 0 DC V_CC
V_i 2 1 AC V_i
R_B 2 3 R_B
R_C 4 5 R_C
Q_1 3 4 0 beta_Q_1
'
```




Typically, when analyzing such circuits, we split up the analysis into a DC-part and an AC-part. To find the DC-equivalent of the circuit above, one can simply call the `dc_eq` function (short for *direct-current-equivalent*).

This function uses lower-level functions such as `short`, `open` and `clean` to modify the given circuit into its DC-equivalent.

```
ELAB.dc_eq(circuit);
circuit.list
```

 
```
ans =
'V_BB 1 0 DC V_BB
V_CC 4 0 DC V_CC
R_B 1 2 R_B
R_C 3 4 R_C
Q_1 2 3 0 beta_Q_1
'
```



Similarly, the program can convert the given circuit into its AC-equivalent.

```
circuit = Circuit('circuits/bjt_cs_amp.txt');
ELAB.ac_eq(circuit);
circuit.list
```
 
```
ans =
'V_i 1 0 AC V_i
R_B 1 2 R_B
R_C 3 0 R_C
Q_1 2 3 0 beta_Q_1
'
```




From the AC-equivalent, you can model the transistor as linear elements, using the `hpi` (hybrid-pi) function, which can either assume the circuit will operate in low-frequency "lf" or high-frequency "hf". We can use the `clone` function to preserve the AC-equivalent, if needed later. The third parameter determines whether the modeller will account for the early effect.

```
circuit = Circuit('circuits/bjt_cs_amp.txt');
ELAB.hybrid_pi(circuit, 'lf', true);
```

```
circuit.list
```

 
```
ans =  
'V_i 1 0 AC V_i  
R_B 1 2 R_B  
R_C 3 0 R_C  
R_pi_Q_1 2 0 R_pi_Q_1  
R_o_Q_1 3 0 R_o_Q_1  
G_Q_1 3 0 2 0 G_Q_1  
,
```



Of course we may also simplify this circuit. The simplifier takes into account that a dependent source relies on the voltage across R_π and so does not simplify the series $R_B + R_\pi$.

```
ELAB.simplify(circuit);  
circuit.list
```
 
```
ans =  
'V_i 1 0 AC V_i  
R_B 1 2 R_B  
R_pi_Q_1 2 0 R_pi_Q_1  
R_eq1 3 0 (R_C*R_o_Q_1)/(R_C+R_o_Q_1)  
G_Q_1 3 0 2 0 G_Q_1  
,
```



```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.225215 sec).

```
circuit.symbolic_node_voltages
```

```
ans =  

$$\begin{pmatrix} v_1 = V_i \\ v_2 = \frac{R_{\pi,Q,1} V_i}{R_B + R_{\pi,Q,1}} \\ v_3 = -\frac{G_{Q,1} R_{eq1} R_{\pi,Q,1} V_i}{R_B + R_{\pi,Q,1}} \end{pmatrix}$$

```

```
ELAB.ec2sd(circuit,1,3)
```

Symbolic transfer function calculated successfully (3.164900e-03 sec).
ans =

$$\frac{v_3}{v_1} = -\frac{G_{Q,1} R_{eq1} R_{\pi,Q,1}}{R_B + R_{\pi,Q,1}}$$

```
circuit = Circuit('circuits/bjt_cs_amp.txt');  
ELAB.hybrid_pi(circuit,'hf', true);  
circuit.list
```


```
ans =  
'V_i 1 0 AC V_i  
R_B 1 2 R_B  
R_C 3 0 R_C  
R_pi_Q_1 2 0 R_pi_Q_1  
R_mu_Q_1 2 3 R_mu_Q_1  
R_o_Q_1 3 0 R_o_Q_1  
C_pi_Q_1 2 0 C_pi_Q_1  
C_mu_Q_1 2 3 C_mu_Q_1  
G_Q_1 3 0 2 0 G_Q_1  
,
```

2. MOSFETs

All the same functionality exists for circuits containing MOSFET transistors. To illustrate this, we load in this circuit.


```
circuit = Circuit('circuits/mos_cs_amp.txt');  
circuit.list
```
 
```
ans =  
'V_i 1 0 AC V_i  
V_DD 3 0 DC V_DD  
R_D 2 3 R_D  
R_G 1 2 R_G  
R_L 2 0 R_L  
M_1 1 2 0 100  
,
```



```
ELAB.hybrid_pi(circuit,'lf', true);  
circuit.list
```
 
```
ans =
'V_i 1 0 AC V_i
R_D 2 0 R_D
R_G 1 2 R_G
R_L 2 0 R_L
R_o_M_1 2 0 R_o_M_1
G_M_1 2 0 0 1 G_M_1
,
```



As this circuit contains three resistors in parallel, we may want to simplify the circuit for further analysis.

```
ELAB.simplify(circuit);
circuit.list
```

```
ans =
'V_i 1 0 AC V_i
R_G 1 2 R_G
R_eq1 2 0 (R_D*R_L*R_o_M_1)/(R_D*R_L+R_D*R_o_M_1+R_L*R_o_M_1)
G_M_1 2 0 0 1 G_M_1
,
```

```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.174017 sec).

```
ELAB.ec2sd(circuit,1,2)
```

Symbolic transfer function calculated successfully (3.558700e-03 sec).

```
ans =
v2/v1 = (R_eq1 (G_M_1 R_G + 1)) / (R_G + R_eq1)
```

3. Numerical evaluation

If there are numerical values available, the program is also able to incorporate these into the modelling of the transistor. We reload the the common-source amplifier with biasing, but this time with numerical values.

```
circuit = Circuit('circuits/bjt_cs_amp_num.txt');
circuit.list
```

```
ans =
'V_BB 1 0 DC 3
V_CC 5 0 DC 10
V_i 2 1 AC V_i
R_B 2 3 100000
R_C 4 5 3000
Q_1 3 4 0 100
,
```

```
circuit = ELAB.biasing(circuit);
```

Symbolic analysis successful (0.307091 sec).

Numerical evaluation successful (0.0570216 sec).

$$I_{V, BE, Q, 1} = 2.3e-5$$

In this case, the biasing/base current is $I_B = 23\mu A$, so the collector current is $I_C = \beta I_B = 2.3mA$. These values are stored in their corresponding transistors, and can be utilized by the hybrid-pi function. This time, we neglect the early effect.

```
ELAB.hybrid_pi(circuit, 'lf', false);  
circuit.list
```

```
ans =  
  'V_i 1 0 AC V_i  
  R_B 1 2 100000  
  R_C 3 0 3000  
  R_pi_Q_1 2 0 1130.4347826086958178137709958459  
  G_Q_1 3 0 2 0 0.088461538461538448576407565561762  
,
```

As can be seen from the netlist, the elements used for the hybrid-pi model has been given numerical values. The voltage-controlled-current-source transconductance is $g_m = 88.5 mA/V$, and the resistance over which the controlling voltage is, has been calculated to be $R_\pi = 1130\Omega$.

We can now treat it as any other linear circuit, like finding the symbolic transfer function.

```
ELAB.ec2sd(circuit, 1, 3)
```

Symbolic analysis successful (0.219763 sec).
Symbolic transfer function calculated successfully (2.268344e-01 sec).
ans =

$$\frac{v_3}{v_1} = -\frac{G_{Q,1} R_C R_{\pi, Q,1}}{R_B + R_{\pi, Q,1}}$$

Or evaluating the transfer function to check the gain.

```
ELAB.ec2tf(circuit, 1, 3)
```

Numerical evaluation successful (0.0642584 sec).
Transfer function object created successfully (7.878930e-02 sec).

```
ans =  
  
-2.966
```

Static gain.

More examples

```
circuit = Circuit('circuits/bjt_complex_amp.txt');  
circuit.list
```

```
ans =  
  'V_cc 4 0 DC V_cc  
  V_s 1 0 AC V_s
```

```

R_s 1 2 R_s
R_1 3 4 R_1
R_2 3 0 R_2
R_C 4 5 R_C
R_L 6 0 R_L
C_1 2 3 C_1
C_2 5 6 C_2
Q_1 3 5 0 beta_Q_1

```

```

ELAB.hybrid_pi(circuit, 'lf', true);
circuit.list

```

```

ans =
'V_s 1 0 AC V_s
R_s 1 2 R_s
R_1 3 0 R_1
R_2 3 0 R_2
R_C 0 4 R_C
R_L 5 0 R_L
R_pi_Q_1 3 0 R_pi_Q_1
R_o_Q_1 4 0 R_o_Q_1
C_1 2 3 C_1
C_2 4 5 C_2
G_Q_1 4 0 3 0 G_Q_1

```

```

ELAB.simplify(circuit);
circuit.list

```

```

ans =
'V_s 1 0 AC V_s
R_s 1 2 R_s
R_L 5 0 R_L
R_eq1 0 4 (R_C*R_o_Q_1)/(R_C+R_o_Q_1)
R_eq2 3 0 (R_1*R_2*R_pi_Q_1)/(R_1*R_2+R_1*R_pi_Q_1+R_2*R_pi_Q_1)
C_1 2 3 C_1
C_2 4 5 C_2
G_Q_1 4 0 3 0 G_Q_1

```

```

circuit.Resistors(3).resistance

```

```

ans =

$$\frac{R_C R_{o,Q,1}}{R_C + R_{o,Q,1}}$$


```

```

circuit.Resistors(4).resistance

```

```

ans =

$$\frac{R_1 R_2 R_{\pi,Q,1}}{R_1 R_2 + R_1 R_{\pi,Q,1} + R_2 R_{\pi,Q,1}}$$


```

