


Simplifying circuits

ELAB can recursively simplify your circuit, updating the entire circuit object in the process.

We start by loading a circuit from a text file and displaying its netlist. This circuit is arbitrary and could be of any size and shape. The circuit is then analyzed and some results are displayed.

```
circuit = Circuit('circuits/passive/c9_series_parallel.txt');  
circuit.list
```
 
```
ans =  
'V1 1 0 AC 10  
R1 1 2 1000  
R2 2 0 2000  
R3 2 0 2000  
R4 1 2 3000  
R5 1 0 1000  
C1 1 0 2  
C2 0 1 3  
,
```



```
ELAB.analyze(circuit)
```

Symbolic analysis successful (0.382734 sec).

```
circuit.symbolic_node_voltages
```

```
ans =  


$$\begin{pmatrix} v_1 = V_1 \\ v_2 = \frac{R_2 R_3 V_1 (R_1 + R_4)}{R_1 R_2 R_3 + R_1 R_2 R_4 + R_1 R_3 R_4 + R_2 R_3 R_4} \end{pmatrix}$$

```

We then simplify the circuit and repeat the process. Notice, that the naming and orientation of individual elements are accounted for.

```
ELAB.simplify(circuit);  
circuit.list
```
 
```
ans =  
'V1 1 0 AC 10  
Req1 1 0 7000/11  
Ceq1 1 0 5  
,
```



ELAB recursively simplified the series and parallel resistors and capacitors, calculating their new values and giving them new names. Since all the resistors and capacitors can be reduced to a single resistor and capacitor in parallel, the node voltage at node 1 is simply the source voltage.

```
ELAB.analyze(circuit)
```

```
Symbolic analysis successful (0.127301 sec).
```

```
circuit.symbolic_node_voltages
```

```
ans = v1 = V1
```

Let's check if it was done right. From the pre-simplify diagram, we see that the resistors simplify to:

$$\begin{aligned} R_{eq1} &= ((R_1 || R_4) + (R_2 || R_3)) || R_5 \\ &= \frac{\left(\left(\frac{1k\Omega \cdot 3k\Omega}{1k\Omega + 3k\Omega} \right) + \left(\frac{2k\Omega \cdot 2k\Omega}{2k\Omega + 2k\Omega} \right) \right) \cdot 1k\Omega}{\left(\left(\frac{1k\Omega \cdot 3k\Omega}{1k\Omega + 3k\Omega} \right) + \left(\frac{2k\Omega \cdot 2k\Omega}{2k\Omega + 2k\Omega} \right) \right) + 1k\Omega} \\ &= 7k\Omega/11 \end{aligned}$$

And the capacitors simplify to:

$$\begin{aligned} C_{eq1} &= C_1 || C_2 \\ &= C_1 + C_2 \\ &= 5 \end{aligned}$$

ELABorate can simplify series and parallels of any 2-terminal element.